



Total Pages : 6

B.Sc./3rd Sem/COS/25(NEP)

2025

3rd Semester Examination (CCFUP : NEP)

COMPUTER SCIENCE

Paper : MI 3-T (Minor)

(Digital Logic)

Full Marks : 60

Time : Three Hours

The figures in the margin indicate full marks.

*Candidates are required to give their answers
in their own words as far as practicable.*

Group - A

Answer any *ten* questions.

2×10=20

1. Represent $(-12)_{10}$ in 2's and 1's complement form.
2. What do you mean by self-complementing code?
3. Subtract $(1100100 - 1001101)$ using 2's complement.
4. Write the BCD equivalent of $(45)_{10}$.
5. What is Gray code and why is it called a unit-distance code?
6. Define De Morgan's law.
7. Reduce $A'B'C' + A'B'C + A'BC + A'BC' + AB'C + ABC$.

P.T.O.

(2)



8. What is propagation delay?
9. What is minterm and SOP?
10. What do you mean by triggering of flip-flop?
11. Differentiate between positive clock edge-triggered and negative-clock edge triggered.
12. What is synchronous counter?
13. Define half adder and write its Boolean expression.
14. What is a multiplexer?
15. What is serial register?

Group - B

Answer any *four* questions.

5×4=20

16. Find the MSOP representation for $F(A, B, C, D, E)$
 $= \Sigma(1, 4, 6, 10, 20, 22, 24, 26) + d(0, 11, 16, 27)$
using K-map.
17. Draw and explain 3 to 8 line decoder.
18. Define full adder. Design a full adder using minimum
number of NAND gates only. 1+4
19. Explain the working of a 4 : 1 multiplexer with truth
table.
20. Draw and explain the logic circuit of an unclocked SR
flip-flop.
21. Design a 4-bit Parallel In Serial Out (PISO) shift register.

(3)

Group - C

Answer any *two* questions. $10 \times 2 = 20$

22. Design and explain about 2-bit Magnitude Comparator.
Design the combinational circuit binary to Gray code converter. $5+5$
23. How does a JK flip-flop differs from an SR flip-flop in its basic operations? Explain. What is master-slave flip-flop? Explain master-slave JK flip-flop. $3+2+5$
24. Design 8 : 1 multiplexer using NAND gates only. Explain Mod-5 counter. $5+5$
25. Describe BCD to excess-3 Code Conversion with truth table and logic diagram. What do you mean by half subtractor and full subtractor? Design a half subtractor using only NOR gates. $5+2+3$

বঙ্গানুবাদ

বিভাগ - ক

যে-কোনো দশটি প্রশ্নের উত্তর দাও : $2 \times 10 = 20$

- ১। $(-12)_{10}$ কে 2 এবং 1 এর পরিপূরক আকারে উপস্থাপন করো।
- ২। স্ব-পরিপূরক কোড বলতে তুমি কী বোঝো?
- ৩। 2-এর পরিপূরক ব্যবহার করে $(1100100 - 1001101)$ বিয়োগ করো।

P.T.O.

(4)

- ৪। $(45)_{10}$ -এর BCD সমমান বাহির করো।
- ৫। Gray code কী? কেন ইহাকে unit-distance code বলা হয়?
- ৬। ডিমরগানের সূত্র (De Morgan's Law) সংজ্ঞায়িত করো।
- ৭। $A'B'C' + A'B'C + A'BC + A'BC' + AB'C + ABC$ হ্রাস করো।
- ৮। প্রসারণ বিলম্ব (propagation delay) কী?
- ৯। মিনটার্ম এবং SOP কী?
- ১০। ফ্লিপ-ফ্লপের ট্রিগারিং বলতে কী বোঝো?
- ১১। পজিটিভ ক্লক এজ-ট্রিগারড এবং নেগেটিভ-ক্লক এজ ট্রিগারডের মধ্যে পার্থক্য কী?
- ১২। সিক্সোনাস কাউন্টার কী?
- ১৩। Half adder-এর সংজ্ঞা দাও এবং এর Boolean expression টি লেখো।
- ১৪। Multiplexer কী?
- ১৫। সিরিয়াল রেজিস্টার কী?

বিভাগ - খ

যে-কোনো চারটি প্রশ্নের উত্তর দাও : $৫ \times ৪ = ২০$

- ১৬। K-মানচিত্র ব্যবহার করে $F(A, B, C, D, E) = \Sigma(1, 4, 6, 10, 20, 22, 24, 26) + d(0, 11, 16, 27)$ -এর জন্য MSOP উপস্থাপনা খোঁজো।

(5)

১৭। 3 থেকে 8 লাইন ডিকোডার আঁকো এবং ব্যাখ্যা করো।

১৮। পূর্ণ অ্যাডার সংজ্ঞায়িত করো। কেবলমাত্র ন্যূনতম সংখ্যক NAND গেট ব্যবহার করে একটি পূর্ণ অ্যাডার ডিজাইন করো।

১+৪

১৯। 4 : 1 multiplexer এর কার্য পদ্ধতি ও ইহার Truth Table ব্যাখ্যা করো।

২০। একটি আনক্লকড SR ফ্লিপ-ফ্লপের লজিক সার্কিট আঁক এবং ব্যাখ্যা করো।

২১। একটি 4-বিট প্যারালাল ইন সিরিয়াল আউট (PISO) শিফট রেজিস্টার ডিজাইন করো।

বিভাগ - গ

যে-কোনো দু'টি প্রশ্নের উত্তর দাও : $১০ \times ২ = ২০$

২২। 2-বিট ম্যাগনিটিউড কম্প্যারেটর ডিজাইন এবং ব্যাখ্যা করো? কস্টনেশনাল সার্কিট বাইনারি থেকে গ্রে কোড কনভার্টার ডিজাইন করো।

৫+৫

২৩। একটি JK ফ্লিপ-ফ্লপের তার মৌলিক ক্রিয়াকলাপে SR ফ্লিপ-ফ্লপ থেকে কীভাবে আলাদা? ব্যাখ্যা করো। মাস্টার-স্লেভ ফ্লিপ-ফ্লপ কী? মাস্টার স্লেভ JK ফ্লিপ-ফ্লপ ব্যাখ্যা করো।

৩+২+৫

২৪। শুধুমাত্র NAND গেট ব্যবহার করে একটি 8 : 1 মাল্টিপ্লেক্সার তৈরি করো। Mod-5 কাউন্টার ব্যাখ্যা করো।

৫+৫

P.T.O.

২৫। Truth টেবিল এবং লজিক ডায়াগ্রাম দিয়ে BCD থেকে Excess-3 কোড রূপান্তর বর্ণনা করো। Full subtractor এবং Half subtractor বলতে তুমি কী বোঝো? শুধুমাত্র NOR গেট ব্যবহার করে একটি Half subtractor ডিজাইন করো।

৫+২+৩
